

# Design a 4-bit ALU

Group: 4 CSE460 Lab Section 9

ATHAR NOOR MOHAMMAD RAFEE

DEPT: CSE

ID: 20101396

Section: 9L

noor.mohammad.rafee@g.bracu.ac.bd

A.S.M MAHABUB SIDDIQUI

DEPT: CSE

ID: 20301040

Section: 9L

asm.mahabub.siddiqui@g.bracu.ac.bd

Ayon Das

DEPT: CSE)

ID: 20301099

Section: 9L

ayon.das@g.bracu.ac.bd

MD. SAKIB

DEPT: CSE

ID: 20301180

Section: 9L

md.sakib1@g.bracu.ac.bd

MOHAMMED INZAM UL AZAM

DEPT: CSE

ID:20101144

Section: 09L

email address or ORCID

**Abstract**—This project presents the design and implementation of a 4-bit Arithmetic Logic Unit (ALU). The ALU performs arithmetic and logical operations on two 4-bit inputs and produces a 4-bit output. The design is implemented using Verilog hardware description language and simulated using timing function. The ALU supports basic arithmetic operations such as addition and subtraction, as well as logical operations such as ADD, NAND, and XNOR as per requirements of the project. Overall, this project demonstrates the design and implementation of a simple but functional sequential ALU using Verilog HDL.

**Index Terms**—ALU, Verilog, arithmetic, logic, simulation

## I. INTRODUCTION

This report presents the design and implementation of a 4-bit ALU using Verilog HDL and Quartus II software. The ALU was designed to perform various arithmetic and logical operations such as addition, subtraction, bitwise AND, bitwise OR, and bitwise XOR. The design consists of various modules such as the Adder, Subtractor, and logic gates which were generated based on the verilog code. In this report, we provide a detailed description of the design and implementation process, including the Verilog code for each module and the timing diagram for verification. We also discuss the challenges encountered during the design process and how they were overcome. Finally, we present the results of the hardware testing, demonstrating that the ALU is capable of performing the desired operations accurately and efficiently. The design of a 4-bit ALU is an essential component in digital circuit design, and it is a fundamental building block in many larger circuits and VLSI design.

## II. FINITE STATE MACHINE DESIGN AND IMPLEMENTATION

Finite State Machine (FSM) is a model for designing sequential logic circuits, where the circuit's behavior is determined by a finite number of states, inputs and outputs. In this case, the FSM is designed to implement four different

operations, namely RESET, XNOR, SUB, and ADD on two 4-bit inputs A and B. The way we coded the Verilog code represents the implementation of the FSM, which is designed to perform the above-mentioned arithmetic and logical operations on the given input values. The FSM has four states, which are encoded as 2-bit values, as follows:

- State 0 (2'b00): In this state, the circuit performs the selected operation on the first bit of the input values and transitions to the next state.
- State 1 (2'b01): In this state, the circuit performs the selected operation on the second bit of the input values and transitions to the next state.
- State 2 (2'b10): In this state, the circuit performs the selected operation on the third bit of the input values and transitions to the next state.
- State 3 (2'b11): In this state, the circuit performs the selected operation on the fourth and most significant bit of the input values and transitions back to the initial state.

Before transition, it also sets the values of *zero flag*, *sign flag* and *carry flag*.

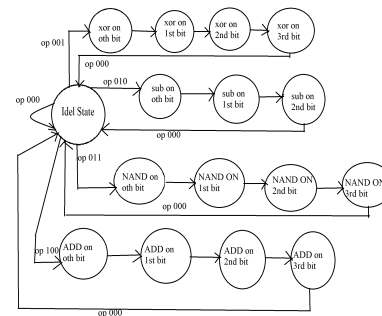


Fig. 1. FSM Diagram

Things are checked and done slightly different based on the *opcode*. It can be observed from the above Fig 1 clearly. The four different operations are implemented using a case statement with *opcode* as the selector. Each operation case statement contains the logic required to perform the operation on the given input values, and update the output values of the circuit accordingly. For example, for the ADD operation, the code first calculates the sum of the LSBs of the input values, adds the carry value to it (initially 0), and assigns the sum and the carry value to the output register C. Then, it updates the zero flag, which is set to 1 if the output is 0, and transitions to the next state which we can see from Fig 1. The outputs of the circuit include C, which stores the result of the operation, carr, which is the carry bit generated during addition or subtraction, sign, which is the sign bit of the output value, and zero, which is set to 1 if the output is zero. Overall, the FSM implementation allows the circuit to perform different arithmetic and logical operations on the given input values, and update the output values based on the operation performed.

### III. VERIFICATION

After implementing the verilog code. We used the timing function to verify the working of the code. Below, we are attaching the screenshots from the timing diagram

#### A. ADD Operation

information for the ADD operation and screenshots from quartus altera's timing diagram.

#### B. SUB Operation

information for the SUB operation and screenshots from quartus altera's timing diagram.

#### C. NAND Operation

information for the NAND operation and screenshots from quartus altera's timing diagram.

#### D. XNOR Operation

information for the XNOR operation and screenshots from quartus altera's timing diagram.

#### E. Full working with reset operation

information for the all operation with reset functionality and screenshots from quartus altera's timing diagram.

### IV. CONCLUSION

In conclusion, we have successfully designed and implemented a 4-bit ALU using finite state machines and *Verilog HDL*. We started by defining the project requirements and selecting the appropriate operations to be implemented. Then, we designed the FSM with four states and carefully defined the transitions and outputs for each state. We also implemented the FSM using Verilog HDL and simulated the design using timing diagram to verify its functionality. The simulation results show that our design works correctly for all the selected operations and input combinations. Finally, this project not only provided

hands-on experience with Verilog HDL programming and digital circuit design, but also reinforced the importance of a systematic approach to problem-solving and the importance of utilizing efficient design strategies.

### APPENDIX

#### A. Verilog HDL Code

```
1 module project(input clk, input [3:0] A,
2   input [3:0] B,
3   input [2:0] opcode, output reg [3:0] C,
4   output reg carr, output reg sign, output
5   reg zero);
6 // Will be using state to indicate state of
7   the machine.
8 reg [1:0] state = 0;
9 always @ (posedge clk) begin
10   case (state)
11     2'b00: begin
12       case (opcode)
13         3'b000: begin
14           C <= 4'b0000; //RESET
15           operation
16           carr <= 1'b0;
17           sign <= 1'b0;
18           zero <= 1'b1;
19         end
20         3'b001: begin //XNOR
21           operation on LSBs
22           C[0] <= ~(A[0] ^ B[0]);
23           zero <= C[0] == 1'b0;
24         end
25         3'b010: begin //SUB
26           operation on LSBs
27           {carr, C[0]} <= B[0] - A
28             [0];
29           zero <= C[0] == 1'b0;
30         end
31         3'b011: begin //NAND
32           operation on LSBs
33           C[0] <= ~(A[0] & B[0]);
34           zero <= C[0] == 1'b0;
35         end
36         3'b100: begin //ADD
37           operation on LSBs
38           {carr, C[0]} <= A[0] + B
39             [0];
40           zero <= C[0] == 1'b0;
41         end
42       endcase
43       state <= 2'b01;
44     end
45     2'b01: begin
46       case (opcode)
47         3'b001: begin //XNOR
48           operation on next bit
49           C[1] <= ~(A[1] ^ B[1]);
50           zero <= zero & (C[1] ==
51             1'b0);
52         end
53         3'b010: begin //SUB
54           operation on next bit
55           {carr, C[1]} <= B[1] - A
56             [1] - carr;
```

```

45         zero <= zero & (C[1] ==
46             1'b0);
47     end
48     3'b011: begin //NAND
49         operation on next bit
50         C[1] <= ~(A[1] & B[1]);
51         zero <= zero & (C[1] ==
52             1'b0);
53     end
54     3'b100: begin //ADD
55         operation on next bit
56         {carr, C[1]} <= A[1] + B
57             [1] + carr;
58         zero <= zero & (C[1] ==
59             1'b0);
60     end
61 endcase
62 state <= 2'b10;
63 end
64 2'b10: begin
65     case (opcode)
66     3'b001: begin //XNOR
67         operation on next bit
68         C[2] <= ~(A[2] ^ B[2]);
69         zero <= zero & (C[2] ==
70             1'b0);
71     end
72     3'b010: begin //SUB
73         operation on next bit
74         {carr, C[2]} <= B[2] - A
75             [2] - carr;
76         zero <= zero & (C[2] ==
77             1'b0);
78     end
79     3'b011: begin //NAND
80         operation on next bit
81         C[2] <= ~(A[2] & B[2]);
82         zero <= zero & (C[2] ==
83             1'b0);
84     end
85     3'b100: begin //ADD
86         operation on next bit
87         {carr, C[2]} <= A[2] + B
88             [2] + carr;
89         zero <= zero & (C[2] ==
90             1'b0);
91     end
92 endcase
93 state <= 2'b11;
94 end
95 2'b11: begin
96     case (opcode)
97     3'b001: begin //XNOR
98         operation on MSBs
99         C[3] <= ~(A[3] ^ B[3]);
100         sign <= C[3];
101         zero <= C == 4'b0000;
102     end
103     3'b010: begin //SUB
104         operation on MSBs
105         {carr, C[3]} <= B[3] - A[3]
106             - carr;
107         sign <= C[3];
108         zero <= C == 4'b0000;
109     end
110     3'b011: begin //NAND
111         operation on MSBs
112         C[3] <= ~(A[3] & B[3]);
113         sign <= C[3];
114         zero <= C == 4'b0000;
115     end
116     3'b100: begin //ADD
117         operation on MSBs
118         {carr, C[3]} <= A[3] + B[3]
119             + carr;
120         sign <= C[3];
121         zero <= C == 4'b0000;
122     end
123 endcase
124 endmodule

```

```

93     if (B[3] < A[3]) begin //
94         if result is negative,
95             take two's complement
96             of result
97         C <= ~C + 4'b0001;
98         sign <= C[3];
99     end
100 end
101 3'b011: begin //NAND
102     operation on MSBs
103     C[3] <=
104         ~(A
105             [3] &
106             B
107             [3]);
108     sign <= C[3];
109     zero <= C == 4'b0000;
110 end
111 3'b100: begin //ADD
112     operation on MSBs
113     {carr, C[3]} <= A[3] + B
114         [3] + carr;
115     sign <= C[3];
116     zero <= C == 4'b0000;
117 end
118 endcase
119 state <= 2'b00;
120 end
121 endcase
122 end
123 endmodule

```

Listing 1. Verilog code for 4-bit ALU