

Design a 4-bit ALU

Group: 4 CSE460 Lab Section 9

ATHAR NOOR MOHAMMAD RAFEE

DEPT: CSE

ID: 20101396

Section: 9L

noor.mohammad.rafee@g.bracu.ac.bd

A.S.M MAHABUB SIDDIQUI

DEPT: CSE

ID: 20301040

Section: 9L

asm.mahabub.siddiqui@g.bracu.ac.bd

Ayon Das

DEPT: CSE

ID: 20301099

Section: 9L

ayon.das@g.bracu.ac.bd

MD. SAKIB

DEPT: CSE

ID: 20301180

Section: 9L

md.sakib1@g.bracu.ac.bd

MOHAMMED INZAM UL AZAM

DEPT: CSE

ID: 20101144

Section: 09L

mohammed.inzam.ul.azam@g.bracu.ac.bd

Abstract—This project presents the design and implementation of a 4-bit Arithmetic Logic Unit (ALU). The ALU performs arithmetic and logical operations on two 4-bit inputs and produces a 4-bit output. The design is implemented using Verilog hardware description language and simulated using timing function. The ALU supports basic arithmetic operations such as addition and subtraction, as well as logical operations such as ADD, NAND, and XNOR as per requirements of the project. Overall, this project demonstrates the design and implementation of a simple but functional sequential ALU using Verilog HDL.

Index Terms—ALU, Verilog HDL, opcode, timing diagram, SUB, XNOR, NAND, ADD, RESET


I. INTRODUCTION

This report presents the design and implementation of a 4-bit ALU using Verilog HDL and Quartus II software. The ALU was designed to perform various arithmetic and logical operations such as **ADDITION**, **SUBTRACTION**, bitwise **AND**, bitwise **OR**, and bitwise **XOR**. The design consists of various modules such as the Adder, Subtractor, and logic gates which were generated based on the verilog code. In this report, we provide a detailed description of the design and implementation process, including the Verilog code for each module and the timing diagram for verification. We also discuss the challenges encountered during the design process and how they were overcome. Finally, we present the results of the hardware testing, demonstrating that the ALU is capable of performing the desired operations accurately and efficiently. The design of a 4-bit ALU is an essential component in digital circuit design, and it is a fundamental building block in many larger circuits and VLSI design.

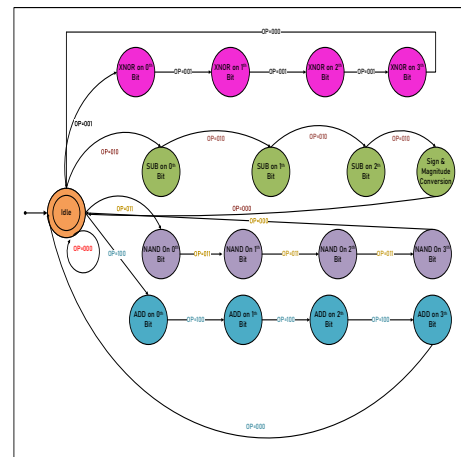II. FINITE STATE MACHINE DESIGN AND IMPLEMENTATION

Finite State Machine (FSM) is a model for designing sequential logic circuits, where the circuit's behavior is determined by a finite number of states, inputs and outputs. In this case, the FSM is designed to implement *five* different

operations, namely RESET, XNOR, NAND, SUB, and ADD on two 4-bit inputs A and B. The way we coded the Verilog code represents the implementation of the FSM, which is designed to perform the above-mentioned arithmetic and logical operations on the given input values. From an high level perspective, The FSM has Four states, which are encoded as 2-bit values, as follows:



of the input values and transitions back to the initial state.

Before transition, it also sets the values of *zero* flag, *sign* flag and *carry* flag.

Things are checked and done slightly different based on the *opcode*. It can be observed from the above Fig 1 clearly. The four different operations are implemented using a *case* statement with *opcode* as the selector. Each operation *case* statement contains the logic required to perform the operation on the given input values, and update the output values of the circuit accordingly. For example, for the **ADD** operation, the code first calculates the SUM of the LSBs of the input values, adds the carry value to it (initially 0), and assigns the SUM and the carry value to the output register **C**. Then, it updates the *zero* flag, which is set to 1 if the output is 0, and transitions to the next state which is **IDLE** state that we can see from Figure 1. The outputs of the circuit include **C**, which stores the result of the operation, *carr*, which is the **carry** bit generated during addition or subtraction, *sign*, which is the sign bit of the output value, and *zero*, which is set to 1 if the output is 0000. Overall, the FSM implementation allows the circuit to perform different arithmetic and logical operations on the given input values, and update the output values based on the operation performed.

III. VERIFICATION

After implementing the verilog code. We used the timing function to verify the working of the code. Below, we are attaching the screenshots from the timing diagram

A. ADD Operation:

Below figure 2 shows the **ADD** operation between two binary $A = 1111$ and $B = 1111$ where the result is stored C sequentially in each clock cycles.

 


Fig. 2. Timing Diagram for ADD Operation

B. SUB Operation

Below figure 3 shows the **SUB** operation between two binary $A = 0111$ and $B = 0111$

 


Fig. 3. Timing Diagram for Sub Operation

NAND and **XNOR** operation are pretty much straight forward. All we had to do is put the equation in the verilog and then the operation performed as expected. Below timing diagram, those operations are attached.

C. NAND Operation

 


Fig. 4. Timing Diagram for NAND Operation

D. XNOR Operation

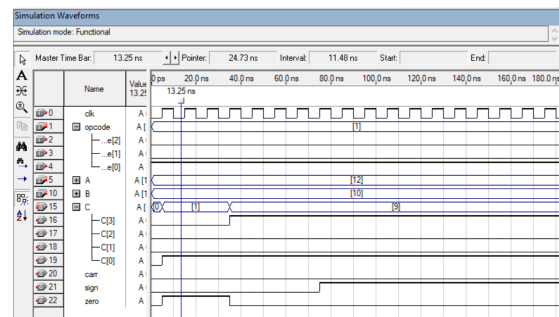


Fig. 5. Timing Diagram for XNOR Operation

E. Multiple Operation With Reset

The below attached Figure 6 shows multiple Operations with **SET** and **RESET** functionality. At first the **SUB** operation is performed between binary number 0111 and 0111. After that, the **opcode** is changed to reset which is 000 during time 40ns to 50ns. Next, the **opcode** was changed to 011 and performed **NANAD** operation during the next 4 clock cycles.

After that the mandatory **RESET** and then **ADD** operation for another 4 cycles.

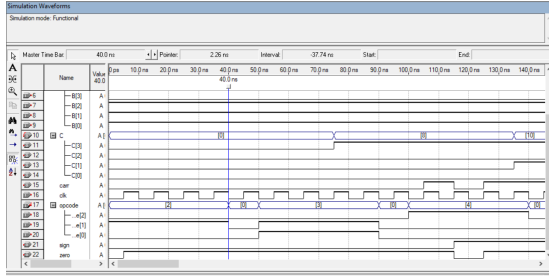


Fig. 6. Timing Daigram with reset

IV. CONCLUSION

In conclusion, we have successfully designed and implemented a 4-bit ALU using finite state machines and *Verilog HDL*. We started by defining the project requirements and selecting the appropriate operations to be implemented. Then, we designed the FSM with four states and carefully defined the transitions and outputs for each state. We also implemented the FSM using Verilog HDL and simulated the design using timing diagram to verify its functionality. The simulation results show that our design works correctly for all the selected operations and input combinations. Finally, this project not only provided hands-on experience with Verilog HDL programming and digital circuit design, but also reinforced the importance of a systematic approach to problem-solving and the importance of utilizing efficient design strategies.

APPENDIX

A. Verilog HDL Code

```
1 module project(input clk, input [3:0] A,
2   input [3:0] B,
3   input [2:0] opcode, output reg [3:0] C,
4   output reg carr, output reg sign, output
5   reg zero);
6 // Will be using state to indicate state of
7   the machine.
8 reg [1:0] state = 0;
9 always @ (posedge clk) begin
10   case (state)
11     2'b00: begin
12       case (opcode)
13         3'b000: begin
14           C <= 4'b0000; //RESET
15           operation
16           carr <= 1'b0;
17           sign <= 1'b0;
18           zero <= 1'b1;
19         end
20         3'b001: begin //XNOR
21           operation on LSBs
22           C[0] <= ~(A[0] ^ B[0]);
23           zero <= C[0] == 1'b0;
24         end
25         3'b010: begin //SUB
26           operation on LSBs
```

```
21   {carr, C[0]} <= B[0] - A
22   [0];
23   zero <= C[0] == 1'b0;
24 end
25 3'b011: begin //NAND
26   operation on LSBs
27   C[0] <= ~(A[0] & B[0]);
28   zero <= C[0] == 1'b0;
29 end
30 3'b100: begin //ADD
31   operation on LSBs
32   {carr, C[0]} <= A[0] + B
33   [0];
34   zero <= C[0] == 1'b0;
35 end
36 endcase
37 state <= 2'b01;
38 end
39 2'b01: begin
40   case (opcode)
41     3'b001: begin //XNOR
42       operation on next bit
43       C[1] <= ~(A[1] ^ B[1]);
44       zero <= zero & (C[1] ==
45       1'b0);
46     end
47     3'b010: begin //SUB
48       operation on next bit
49       {carr, C[1]} <= B[1] - A
50       [1] - carr;
51       zero <= zero & (C[1] ==
52       1'b0);
53     end
54     3'b011: begin //NAND
55       operation on next bit
56       C[1] <= ~(A[1] & B[1]);
57       zero <= zero & (C[1] ==
58       1'b0);
59     end
60     3'b100: begin //ADD
61       operation on next bit
62       {carr, C[1]} <= A[1] + B
63       [1] + carr;
64       zero <= zero & (C[1] ==
65       1'b0);
66     end
67   endcase
68   state <= 2'b10;
69 end
70 2'b10: begin
71   case (opcode)
72     3'b001: begin //XNOR
73       operation on next bit
74       C[2] <= ~(A[2] ^ B[2]);
75       zero <= zero & (C[2] ==
76       1'b0);
77     end
78     3'b010: begin //SUB
79       operation on next bit
80       {carr, C[2]} <= B[2] - A
81       [2] - (carr & ~zero);
82       zero <= zero & (C[2] ==
83       1'b0);
```

```

69         end
70         3'b011: begin //NAND
71             operation on next bit
72             C[2] <= ~(A[2] & B[2]);
73             zero <= zero & (C[2] ==
74                 1'b0);
75         end
76         3'b100: begin //ADD
77             operation on next bit
78             {carr, C[2]} <= A[2] + B
79                 [2] + carr;
80             zero <= zero & (C[2] ==
81                 1'b0);
82         end
83     endcase
84     state <= 2'b11;
85 end
86 2'b11: begin
87     case (opcode)
88     3'b001: begin //XNOR
89         operation on MSBs
90         C[3] <= ~(A[3] ^ B[3]);
91         sign <= C[3];
92         zero <= C == 4'b0000;
93     end
94     3'b010: begin //SUB
95         operation on MSBs
96         {carr, C[3]} <= B[3] - A[3]
97             - carr;
98         sign <= C[3];
99         zero <= C == 4'b0000;
100         if (B[3] < A[3]) begin //
101             if result is negative,
102             take two's complement
103             of result
104             C <= ~C + 4'b0001;
105             sign <= C[3];
106         end
107     end
108     3'b011: begin //NAND
109         operation on MSBs
110         C[3] <=
111             ~(A
112                 [3] &
113                 B
114                 [3]);
115         sign <= C[3];
116         zero <= C == 4'b0000;
117     end
118     3'b100: begin //ADD
119         operation on MSBs
120         {carr, C[3]} <= A[3] + B
121             [3] + carr;
122         sign <= C[3];
123         zero <= C == 4'b0000;
124     end
125 endcase
126     state <= 2'b00;
127 end
128 endcase
129 end
130 endmodule

```

Listing 1. Verilog code for 4-bit ALU